

Roll No.

OLE-24004
B. Tech. 1st Semester
(Common for All Branches)
Examination – April, 2021

BASICS OF ELECTRONICS

Paper : ECE-101-F

Time : Three Hours]

[Maximum Marks : 100

Before answering the questions, candidates should ensure that they have been supplied the correct and complete question paper. No complaint in this regard, will be entertained after examination.

Note : Attempt *five* questions in all, selecting *one* question from each Section. Question No. **1** is **compulsory**. All questions carry equal marks.

1. (a) Explain the necessity of doping.
- (b) Difference between Diffusion and Drift current.
- (c) Explain conditions for oscillation.
- (d) Difference between ON-line and OFF line UPS.
- (e) Write down the characteristics of ideal OP-Amp.
- (f) Why feedback is required ? And where +ve feedback is required.

- (g) What is graticule ?
- (h) Define datch and flip flop.
- (i) Why is the efficiency of SMPS high ?
- (j) Convert Hexa-decimal number $(DFCF)_{16}$ into Octal Number. With procedure. $2 \times 10 = 20$

SECTION – A

2. (a) What is a p-n junction ? Explain the formation of potential barrier in a p-n junction ? 10
- (b) What is meant by biasing of a p-n junction diode ? Why is it necessary ? Also explain the V-I characteristics of junction diode. 10
3. (a) A multistage amplifier employs five stages each of which has a power gain of 30. (i) What is the total gain of the amplifier in db ? (ii) If a negative feedback of 10 db is employed, find the resultant gain. 10
- (b) Explain transistor R-C coupled amplifier with special reference to frequency response, advantages, disadvantages and applications. 10

SECTION – B

4. (a) Explain the principle of Wein bridge Oscillator Circuit. Explain why negative feedback in addition to the usual positive feedback is employed in Wein bridge Oscillator. 10
- (b) Describe the crystal oscillator. What is the advantage of a crystal oscillator over an LC oscillator. 10

5. (a) Describe working principle of inverter and its applications. 10
(b) What is UPS ? Explain in brief UPS ONLINE and OFF LINE mode. 10

SECTION – C

6. (a) Draw the basic block diagram of CRT and explain its working. 10
(b) Describe analog and digital multimeter and its importance and applications. 10
7. (a) What is SR flip-flop ? Give its truth table. Explain how a flip-flop can be obtained by using two single-input NAND gates. Name some other types of flip-flop. 10
(b) Convert the following : $2 \times 5 = 10$
(i) $(8AB4.01)_{16}$ into Octal.
(ii) $(754.32)_8$ into Decimal.
(iii) $(1094.45)_{10}$ into Hexadecimal.
(iv) $(101110011.00)_2$ into Decimal.
(v) $(0.625)_{10}$ into Binary.

SECTION – D

8. (a) Discuss with a neat diagram, a method of realising a 7 segment numeric display using LEDs. 10
(b) Draw a structure of a LED and explain its operation. What are the conditions to be satisfied by the device for emission of visible light ? 10

9. (a) Explain how numeric and alpha numeric characters are displayed using dot matrices. 10
- (b) Differentiate between transmitting and refractive type LCD. Write advantages of LCD display. 10
-