

Roll No. :

Total No. of Questions : 9]

[Total No. of Pages : 3

3350

**B.Tech. (EE) 6th Semester (Supplementary)
Examination, July-2021
(G Scheme)**

POWER ELECTRONICS

Paper-PCC-EE-306-G

Time : Three Hours]

[Maximum Marks : 75

Before answering the questions, candidates should ensure that they have been supplied the correct and complete question paper. No complaint in this regard, will be entertained after examination.

Note :- Attempt *five* questions in all, selecting *one* question from each Section. Question No. 1 is compulsory. All questions carry equal marks.

1. (a) Explain the role of Power Electronics.
- (b) Discuss the characteristic features of GTO.
- (c) Explain dv/dt protection of SCR.

(d) What is meant by Two Pulse Converter ?

(e) List the function of freewheeling diodes in controlled rectifier.

(f) Define derating factor of series connected SCRs. $2\frac{1}{2} \times 6 = 15$

Section-A

2. (a) Compare IGBT and Power Transistor.

(b) Discuss the merits and demerits of Power Electronics System. List some applications of Power Electronics. $7\frac{1}{2}, 7\frac{1}{2}$

3. Explain the construction and characteristics of Power Transistor and discuss important operating regions of power transistor. 15

Section-B

15 each

4. Sketch the V-I characteristics of an SCR and explain latching current, holding current and break over voltage.

5. With a neat circuit diagram and waveforms explain resistor triggering circuit and RC triggering circuit to Turn ON the SCR.

3350_900

(2)

RD-3488

Section-C

6. (a) Draw and explain single phase full wave converter in bridge configuration supplying highly inductive load.

(b) Compare Fully Controlled and Half Controlled Converters. $7\frac{1}{2}, 7\frac{1}{2}$

7. Draw and explain the three phase fully controlled converter operation with RL load and derive the expression for DC output voltage. 15

Section-D

15 each

8. Explain the operation of 120-degree mode three-phase Voltage Source Inverter (VSI).

9. Explain in detail how choppers are classified.

3350_900

(3)

RD-3488