

Roll No. ....

**24007**

**B. Tech. 1st Sem.  
(Common for All Branches)  
Examination – March, 2021**

**ELECTICAL TECHNOLOGY**

Paper : EE-101-F

**Time : Three Hours ] [ Maximum Marks : 100**


*Before answering the questions, candidates should ensure that they have been supplied the correct and complete question paper. No complaint in this regard, will be entertained after examination.*

**Note :** Attempt *five* questions in all, selecting *one* question from each Section. Q. No. 1 is *compulsory*. All questions carry equal marks.


1. (i) Define Mesh, Loop, Node, Bilateral Network and Active Network. 5
- (ii) Define power factor. What is physical significance of power factor. 5
- (iii) Derive e.m.f. equation of D.C. generator. 5
- (iv) Explain the terms controlling torque and damping torque. 5

**SECTION - A**

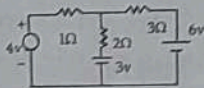2. State and explain Thevenin's theorem. Find the value of current through  $3\Omega$  by using Thevenin's theorem in given network. 20



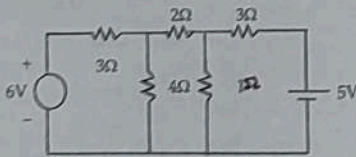3. State Kirchoff's current law. Solve the given network by using nodal analysis and find value of current through  $2\Omega$  resistance. 20



**SECTION - B**

4. Derive the mathematical equation of Average value of sinusoidal AC signal. 20
5. Write short note on : 20
- (a) Series Resonance
- (b) Active power

24007- (P-3)(Q-8)(21) (2)

- (c) Reactive Power
- (d) Earthing

**SECTION - C**

6. Explain, how the rotor of 3- $\phi$  induction motor rotate ? 20
7. Discuss Double field revolving theory in detail. 20

**SECTION - D**

8. Draw and explain equivalent circuit of 1- $\phi$  transformer in detail with phasor diagram on inductive load. 20
9. Derive the equation of power in 3- $\phi$  delta connected system. 20

24007- (P-3)(Q-8)(21) (3)