

Roll No. ....

**OLE-24043**  
**B. Tech. 3rd Sem. (IT)**  
**Examination – April, 2021**

**DIGITAL ELECTRONICS**

**Paper : EE-204-F**

*Time : Three Hours ]*

*[ Maximum Marks : 100*

---

*Before answering the questions, candidates should ensure that they have been supplied the correct and complete question paper. No complaint in this regard, will be entertained after examination.*

---

**Note :** Attempt *five* questions in all, selecting *one* question from each Section. Question No. **1** is *compulsory*. All questions carry equal marks.

1. (a) Difference between counters and registers.
- (b) Hamming codes.
- (c) Design a single bit magnitude comparator to compare two alphabets C and D.
- (d) State the difference between Mealy and Moore state machines.
- (e) How a D flip-flop convert into T flip-flop.

(f) Discuss free state assignment.

(g) Simply :

$$F = \overline{A}(\overline{B} + \overline{C}) + BC + A\overline{C}$$

(h) Error detecting and correcting codes.  $2.5 \times 8 = 20$

## SECTION – A

2. (a) Minimize the function using Quine-Mcluskey method.

$$Y(ABCDE) = \Sigma(0, 1, 4, 7, 9, 11, 21, 26, 30) + d(3, 12, 18)$$

10

(b) Explain how will you obtain Boolean expression for a logic diagram and logic diagram for a Boolean expression with the help of examples. 10

3. (a) (i) Multiply  $(110.10)_2$  by  $(11.01)_2$ . 10

(ii) Convert  $(10101011)_2$  to its gray code.

(iii) Add  $+112_{10}$  and  $+65_{10}$  using  $2_s$  compliment arithmetic.

(iv) Add the following hexa decimal number :

$$(i) 1256 + 3DFF \quad (ii) 21F + BFC$$

(b) Solve the functions using k-map. For SoPsPoS.

$$f(ABCD) = \pi(0, 2, 3, 5, 8, 9, 11)$$

10

## SECTION – B


4. (a) What do you mean by Multiplexer ? Realize 32:1 Multiplexer using two 16:1 Multiplexer. 10
- (b) What is an adder ? Explain its logic diagram with truth table. 5
- (c) Differentiate combinational and sequential logic circuits. 5
5. (a) Explain the function of Demultiplexer in detail with its diagram. 10
- (b) What are encoders and where are they used ? Draw and explain a decimal to BCD encoder. 10

## SECTION – C

6. (a) What are counters ? How we use them in digital system ? Explain asynchronous and synchronous counters with diagrams. 10
- (b) Design a shift register counter to generate a sequence length of 8 having self start feature. 10
7. (a) Explain the working of Master Slave JK flip flop and what is race-around condition. How it can be removed. 10
- (b) Design a Mod-5 Synchronous counter using J-K flip-flop and draw its state diagram. 10

## SECTION – D

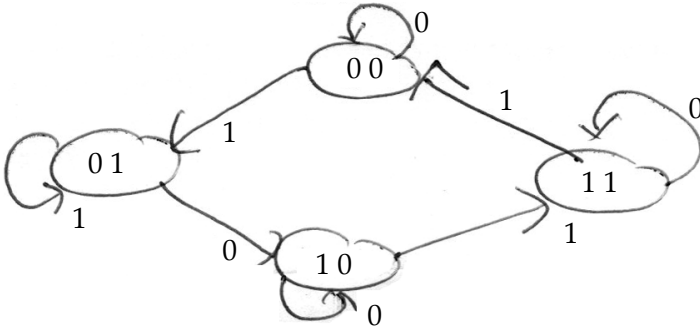8. (a) Explain different types of Hazards in combinational circuit. 10
- (b) For state diagram in figure, obtain the state table and design the circuit using minimum number of JK flip flops. 10



9. (a) Differentiate between RAM and ROM including their advantages, disadvantages and applications. 10
- (b) Write a short note on the followings :
- (i) Asynchronous sequential logic.
  - (ii) Reduction of states.
  - (iii) ASMs. 10