

Roll No. ....

**OLE-24025**  
**B. Tech. 3rd Sem. (EEE)**  
**Examination – April, 2021**

**NETWORK THEORY**

**Paper : EE-203-F**

*Time : Three Hours ]*

*[ Maximum Marks : 100*

---

*Before answering the questions, candidates should ensure that they have been supplied the correct and complete question paper. No complaint in this regard, will be entertained after examination.*

---


**Note :** Attempt *five* questions in all, selecting *one* question from each Section. Question No. 1 is *compulsory*. All questions carry equal marks.

1. (i) What are the difference between loop and nodal analysis ? 5 × 4 = 20
  
- (ii) Drive the expression for series interconnection of two port network.
  
- (iii) What are the properties of Hurwitz polynomial ?


(iv) Explain the concept of duality in network.

### SECTION – A

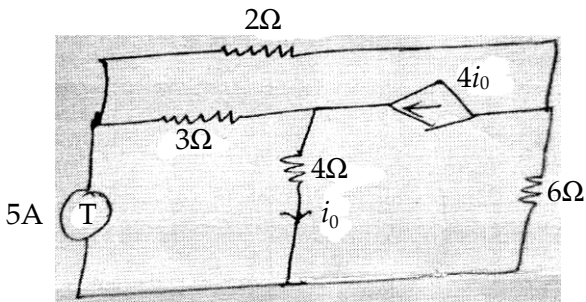2. Find voltage at the three non-reference node for the circuit as shown below : 20



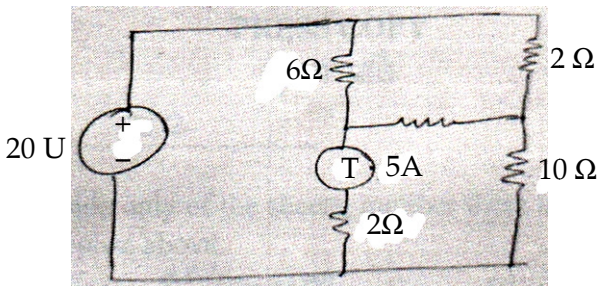3. Determine  $I_1$ ,  $I_2$  and  $I_3$  using mesh analysis for the circuit as shown below : 20



## SECTION – B

4. Explain Thevenin's theorem with suitable example. 20
5. Explain the various interconnection of two port network. 20

## SECTION – C

6. (i) Check whether the following polynomial are Hurwitz or not ? 20

$$P(S) = 6S^5 + 5S^4 + S^3 + 2S^2 + 3S + 18$$


- (ii) Write down the properties of LC function.

7. Check whether following function is p.r.f or not ? 20

$$F(s) = (5S^2 + 9S + 3)/(S^3 + 4S^2 + 7S + 9)$$

## SECTION – D

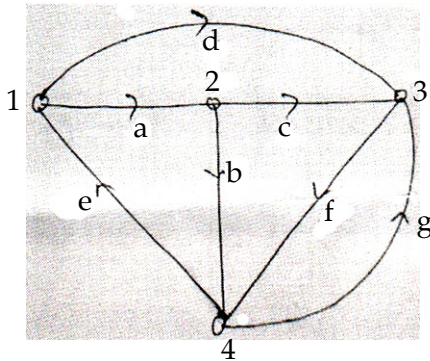8. Develop tie set and cut set matrix for the graph shown below : 20



9. Drive the expression for synthesis of  $Y_{21}$  with 1 ohm termination and also synthesize the network with suitable example. 20
-