

Roll No. ....

## OLE-3038

### B. Tech 3rd Semester (ECE) Examination – April, 2021

#### NETWORK THEORY

Paper :PCC-ECE-211-G

*Time : Three Hours ]*

*[ Maximum Marks :75*

---

*Before answering the questions, candidates should ensure that they have been supplied the correct and complete question paper. No complaint in this regard, will be entertained after examination.*

---

**Note :** Question No. 1 is *compulsory*. Attempt *five* questions in total selecting *one* question from each Section.


1. (a) Give Applications of Maximum power transfer theorem.
- (b) Define cycle, frequency and time period.
- (c) Discuss difference between series and parallel resonance.

- (d) What is importance of power factor and how it is calculated ?
- (e) Discuss prototype band reject filter.
- (f) Give characteristics of two port network.

$$2.5 \times 6 = 15$$

### SECTION – A

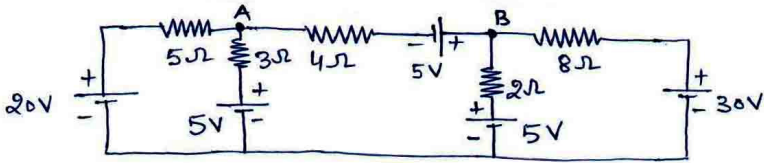2. Find the current supplied by each battery in the circuit shown in fig. by using Node analysis. 15



3. Explain the following theorems : 15
- (a) Norton's theorem
  - (b) Tallegen's theorem.

### SECTION – B

4. Explain steady state response of a network to non-sinusoidal periodic inputs. 15

5. (a) Discuss properties of Laplace transform. 7.5  
(b) Discuss wave form synthesis. 7.5

### SECTION – C

6. Drive an expression for transient response in RLC circuit with DC excitation. 15
7. (a) Explain convolution theorem. 7.5  
(b) Discuss sinusoidal response for pole-zero locations. 7.5

### SECTION – D

8. (a) Discuss short - circuit Admittance parameters. 7.5  
(b) Explain interconnection of two port networks. 7.5
9. Write short notes on : 15  
(a) Analysis & design of prototype high pass filters.  
(b) Graph matrices.
-