

9. (a) Explain the Amplitude Modulation (AM) with the help of suitable block diagram. 10
- (b) Explain the characteristics of wired and wireless transmission medium used in communication. 5

Roll No. ....

**3058**

**B. Tech. 3rd Semester (ME)  
Examination – March, 2021  
BASICS OF ELECTRONICS ENGG.**

Paper : ESC-ECE-207-G

Time : Three Hours ]

[ Maximum Marks : 75

*Before answering the questions, candidates should ensure that they have been supplied the correct and complete question paper. No complaint in this regard, will be entertained after examination.*

**Note :** Attempt *five* questions in all, selecting *one* question from each Unit. Question No. 1 is *compulsory*. All questions carry equal marks.

1. (a) What is a PN junction diode ?
- (b) What do you mean by damping oscillations ?
- (c) What is the function of IC-7805 ? Draw its pin diagram.
- (d) What is the need of feedback in amplifiers ?
- (e) What are universal gates and why ?
- (f) Draw the truth table of a half adder ckt. and its logic diagram.

3058-2350-(P-4)(Q-9)(21)

( 4 )

3058-2350-(P-4)(Q-9)(21)


P. T. O.

UNIT - I

2. (a) What are intrinsic and extrinsic semiconductors? 7.5  
 (b) What is a zener diode? How it is used as a voltage regulator? 7.5
3. (a) Draw and explain the working of a full wave rectifier. 5  
 (b) Find out the expression for rms value and average value of ac voltage obtained from the output of a full wave rectifier. 10

UNIT - II

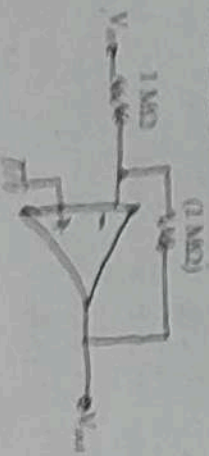4. Draw the O/A diagram using op-amp for : 15  
 (a) Integrator  
 (b) Differentiator
- Also find the expression for the o/p obtained across integrator and differentiator O/A drawn above.
5. (a) What are the effects of negative feedback in case of op-amp? 5  
 (b) Find out the o/p voltage of the amplifier O/A shown below. 5



3058-2550-(P-4)(Q-9)(21) (2)

- (c) Find out the voltage gain of the O/A shown below : 5



UNIT - III

6. (a) What is RC-phase shift oscillator? Draw the circuit diagram. 10  
 (b) What are the advantages and disadvantages of phase shift oscillator? 5
7. (a) What is a crystal oscillator? Draw its equivalent circuit. 8  
 (b) What are the advantages and applications of a crystal oscillator? 7

UNIT - IV

8. (a) What is race around conditions in flip-flop? 5  
 (b) Explain the working of serial in serial out shift register with the help of suitable diagram. 10

3058-2550-(P-4)(Q-9)(21) (3)

P. T. O.