

Roll No.

OLE-24227
B. Tech. 5th Sem. (EEE)
Examination – April, 2021
ANALOG ELECTRONIC CIRCUITS
Paper : EE-305-F

Time : Three hours]

[Maximum Marks : 100

Before answering the questions, candidates should ensure that they have been supplied the correct and complete question paper. No complaint in this regard, will be entertained after examination.

Note : Students have to attempt first common question. which is *compulsory* and *one* question from each of the four Units.

1. (a) Write about the feedback concept and the transfer gain with feedback.
- (b) Discuss general form of oscillator circuit.
- (c) What is the difference between ideal and practical oscillator ?
- (d) Discuss sample and hold circuits. 5 × 4 = 20

UNIT – I

2. (a) Explain RC coupled amplifier. $10 \times 2 = 20$
(b) Discuss multistage CE amplifier.
3. (a) Write about general characteristics of negative feedback amplifiers. $10 \times 2 = 20$
(b) Discuss current series feedback.

UNIT – II

4. Write a note on : $10 \times 2 = 20$
(a) Sinusoidal oscillators
(b) R-C phase shift oscillators
5. Explain : $10 \times 2 = 20$
(a) Wien-bridge oscillator
(b) Crystal oscillator

UNIT – III

6. Write about efficiency & distortion in class B and class C power amplifier. 20
7. (a) Write a note on inverting and non inverting amplifier. 10
(b) Discuss transfer characteristics of a differential amplifier. 10

UNIT – IV

8. Discuss various linear applications of operational amplifiers including scale changer, phase shifter, adder, integrator and differentiator. 20
9. (a) Discuss logarithmic multiplier. 10
- (b) What is a Miller & Bootstrap sweep generator ? 10
-