

9. Explain the following :

- (a) Instruction Cycle
- (b) Instruction Format

8

8

Roll No.

97666

BCA 2nd Semester

Examination – July, 2021

LOGICAL ORGANIZATION OF COMPUTER

Paper : BCA-107

Time : Three hours]

[Maximum Marks : 80

Before answering the questions, candidates should ensure that they have been supplied the correct and complete question paper. No complaint in this regard, will be entertained after examination.

Note : Question No. 1 is compulsory. Attempt other four questions by selecting one question from each Unit. All questions carry equal marks.

1. (a) What is program-controlled I/O technique ?

2×8=16

(b) What is up-down counter ?

(c) What is an Instruction Format ?

(d) What is clocked RS flip-flop ?

(e) What characterizes flash memory ?

(f) Why Master-Slave flip-flop is called so ?

(g) What are applications of ROM ?

(h) What is an IOP ? State its significance.

UNIT - I

2. (a) What do you mean by State Diagrams ? How are these relevant in design of Flip-flops ? Explain. 8

(b) What are Excitation Tables ? How are these relevant ? Draw Excitation Table for RS and JK flip-flop. 8

3. Explain the following :

(a) T Flip-Flop 8

(b) Master-Slave flip-flop 8

UNIT - II

4. (a) What is meant by a universal shift registers ? Design a 4-bit shift register and outline the procedure for serial to parallel conversion and vice-versa. 8

(b) What are synchronous binary counters ? Draw its block diagram and illustrate its operation. 8

5. Explain the following :

(a) Asynchronous Sequential Circuit 8

(b) Modulo-8 Counter 8

UNIT - III

6. (a) What is semiconductor RAM ? How do you design a RAM cell ? Illustrate. 8

(b) What are I/O device controllers ? How these work ? Illustrate their working. 8

7. Explain the following :

(a) Magnetic Disks 8

(b) Characteristics of Memory Cell 8

UNIT - IV

8. (a) What are I/O channels ? How do these work ? Illustrate their working. 8

(b) What are interrupts ? How are these useful ? What is Interrupt structure ? Illustrate. 8